

CPU Control Design

ALU + Regfile + Memory + PC + Control FSM

Which addressing modes should you implement?

- Read the ISA.pdf, as well as the CR16 programmer reference manual on Canvas
- Some addressing modes we have to implement, others are your choice
- **Register mode** (R-type instructions): compulsory
 - ADD Rsrc Rdest: $R_{dest} \leftarrow R_{src} + R_{dest}$
 - Arithmetic, logical, Move: are R-type instructions
 - Make a list of all these instructions

Which addressing modes should you implement?

- **Immediate mode** (I-type instructions): compulsory
 - ADDI Imm Rdest: $R_{dest} \leftarrow \$Imm + R_{dest}$
 - Arithmetic, logical, Move: are included in I-type instructions
 - ISA.pdf shows: ADDI, SUBI, CMPI, ANDI, XORI,..., MOVI
 - They behave similarly as R-type instructions
 - Make a list of all these instructions

Which addressing modes should you implement?

- **Direct/Absolute Addressing mode** (Dir-type instructions): Not compulsory, can do without
 - $\text{ADD } R_{\text{dest}}, [\text{addr}] : R_{\text{dest}} \leftarrow R_{\text{dest}} + [\text{mem addr}]$
 - $[\text{mem addr}]$ = data resides in memory, whose address is “mem addr”
 - Not implemented in CR16
 - More complicated, requires memory access

Which addressing modes should you implement?

- **Indirect Addressing mode** (Ind-type instructions): Compulsory
 - LOAD Rdest, Raddr : $R_{dest} \leftarrow [R_{addr}]$
 - Load data into Rdest, where data resides in memory whose address is stored in Raddr register
 - STOR Rsrc, Raddr: $[Raddr] \leftarrow Rsrc$
 - Store the data of Rsrc into memory at address [Raddr]
 - We will build a Load-Store machine: Use LOAD/STOR to fetch data into regfile, and then perform R-type instructions for computations!


Which addressing modes should you implement?

- **PC-Relative/Displacement Addressing mode** (Rel-type instructions): Compulsory
 - Conditional Branches and Jumps: *e.g.*, “*Bcond disp*”:
 - If condition *cond* is met, branch to memory address ($PC + disp$)
 - $PC \leq PC + disp$
 - ISA.pdf: *disp* = 8-bit 2’s complement integer (bit vector), *disp* is given in the opcode
 - Branch versus Jump: “*Jcond R_{target}*”: Jump to address that is stored in R_{target}
 - If condition is met, then $PC = R_{target}$
 - Condition codes are given on the page 6 in ISA.pdf. You have to implement a few, EQ, NE: Zero flags, CS, CC: Carry, GT, LE: Negative, FS, FC: Overflow


Approach

- First you should implement R-type instructions
 - Design Datapath to support R-type instructions: Program Counter [$PC = PC + 1$]
 - Design FSM
- Then implement Load/Store instructions
 - Augment the Datapath: [$PC = Raddr$]
 - Augment your FSM for Load/Store Instructions
- Finally, include Jumps and Branches

Datapath for R-type Instructions

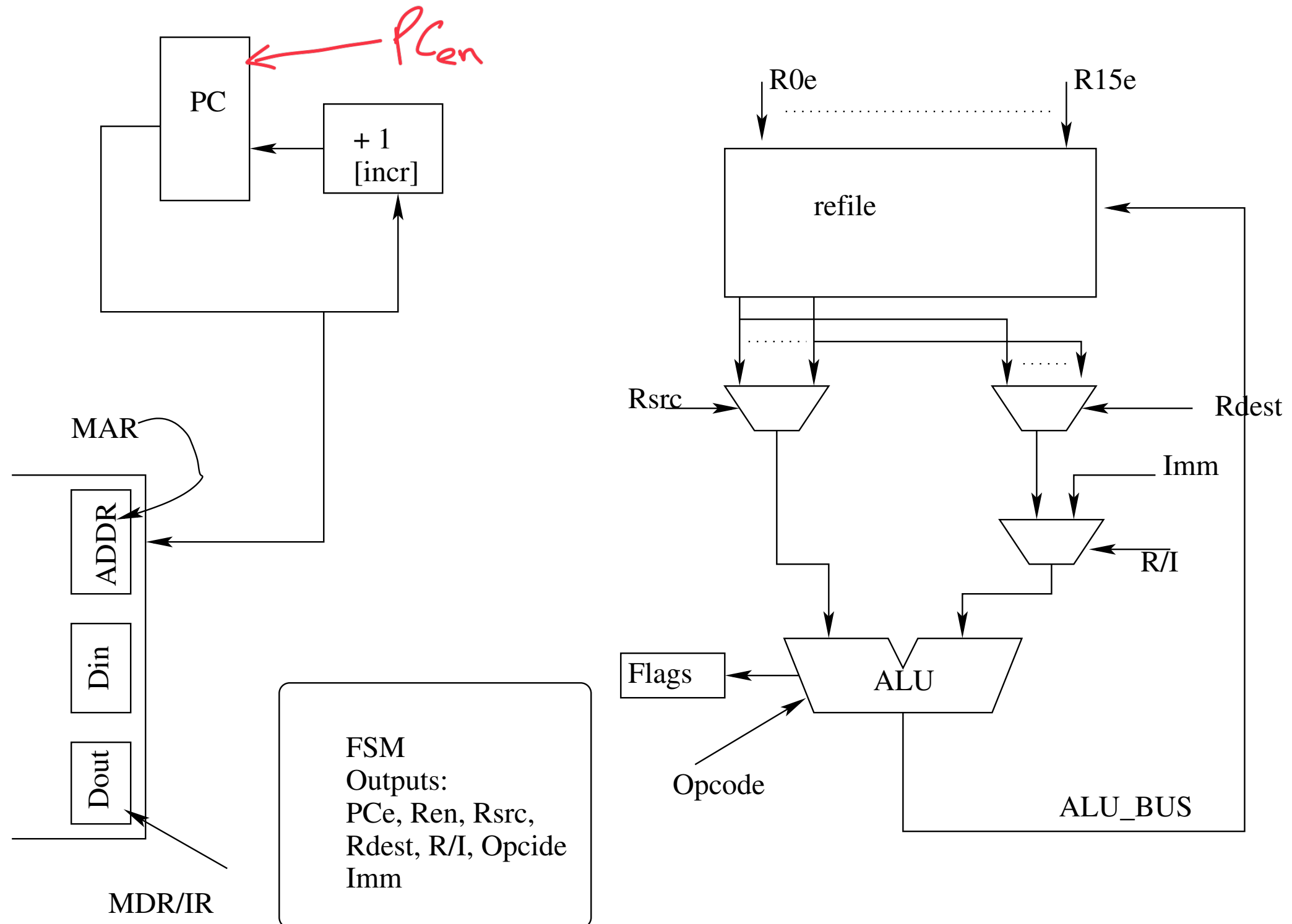


FSM Design for R-type

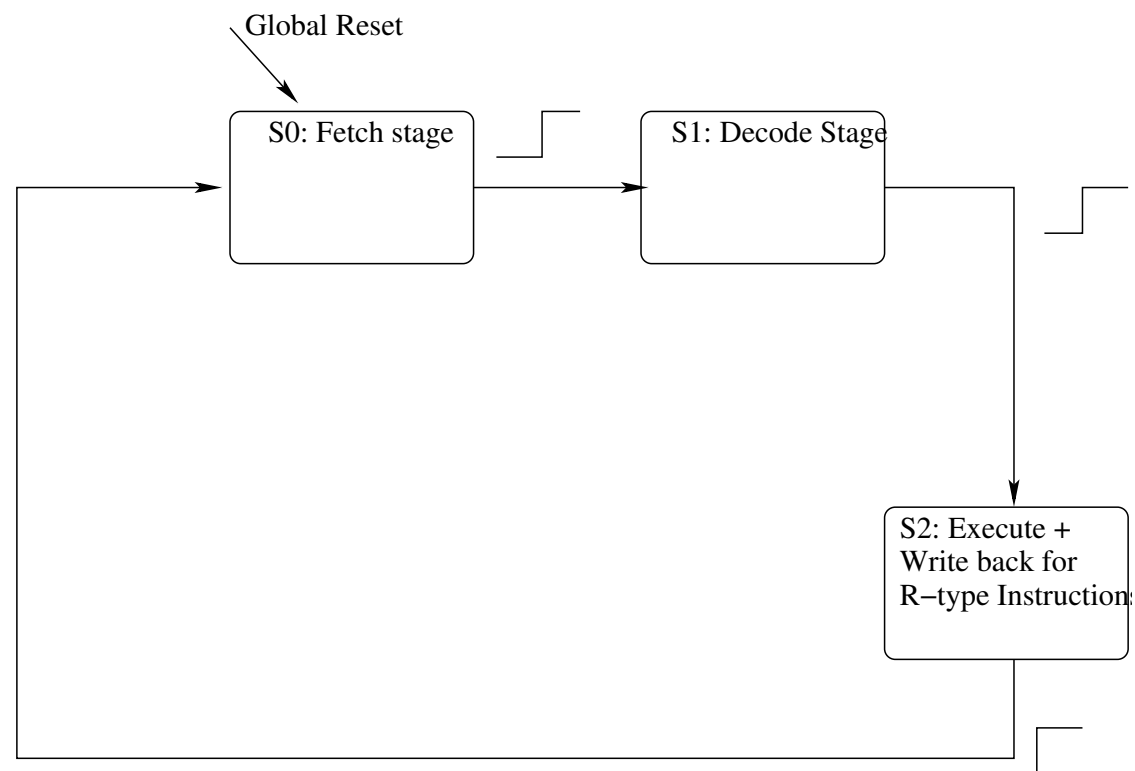

- State S0: $PCe = 0$; $Ren=0$; $Rsrc = 4'bx$; $Rdest=4'bx$; $Opcode = 8'bx$; $R/I = 1'bx$; $Imm=8'bx$
 - Next state = S1
- State S1:
 - If $Opcode = R\text{-type}$, then $NS = S2$
- State S2: **$PCe = 1$**
// Don't write $PC = PC + 1$ in your FSM's logic in Verilog


A More Structural Design

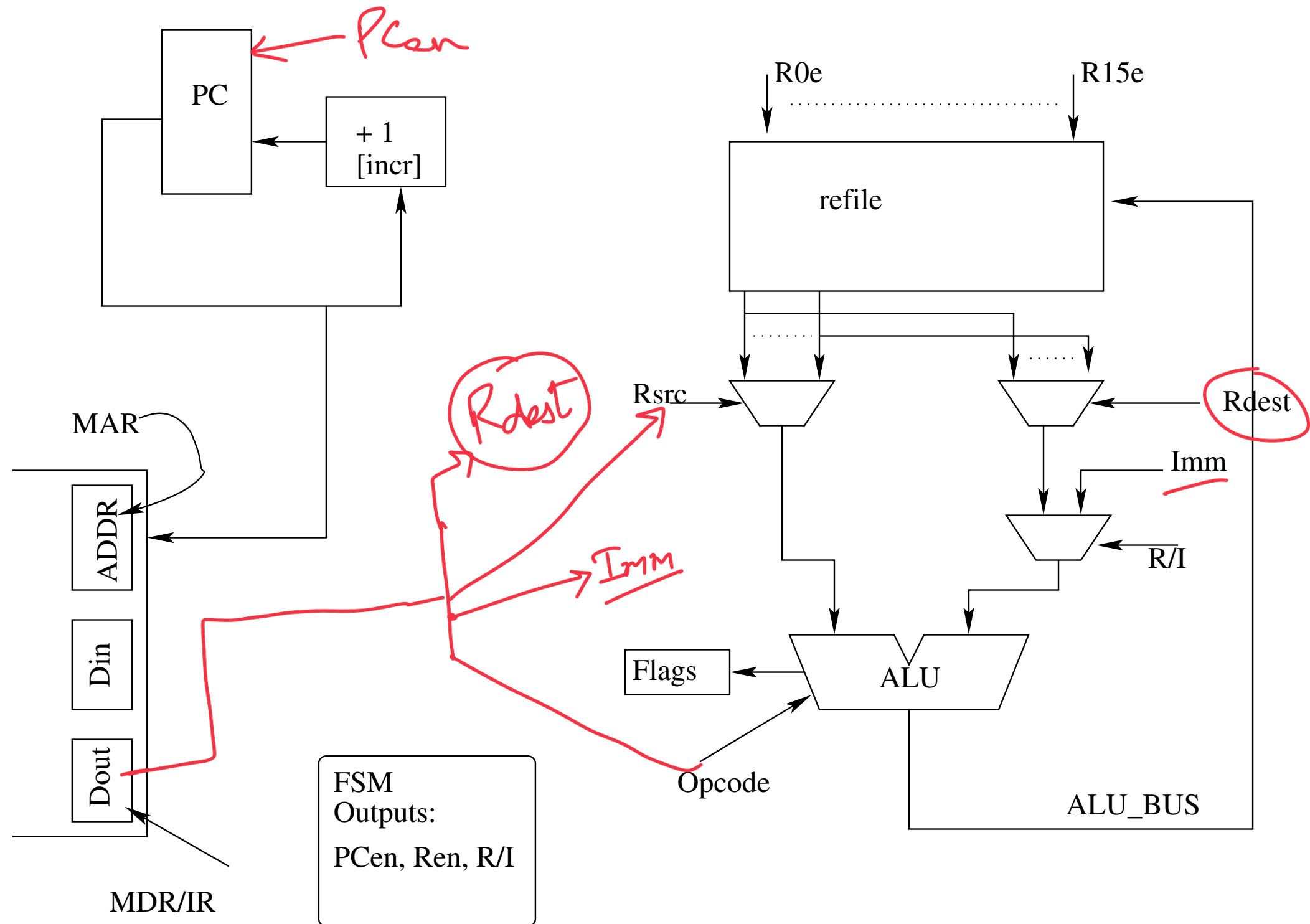


- More structural design, leaner/simpler FSM


Store Instruction

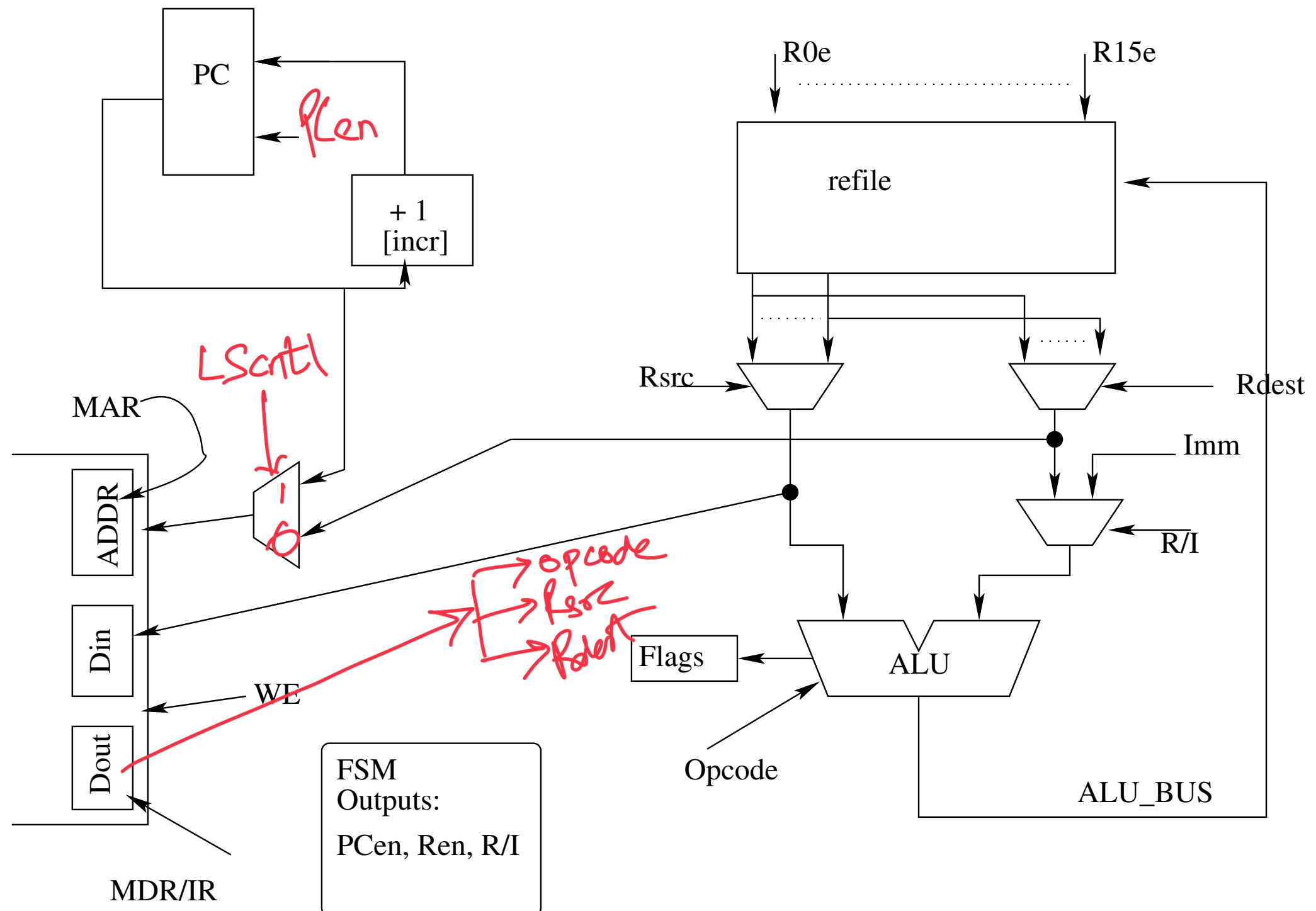- STOR Rsrc Raddr: Store data (in Rsrc) in memory at address given in Raddr



Update your FSM with Store Instruction

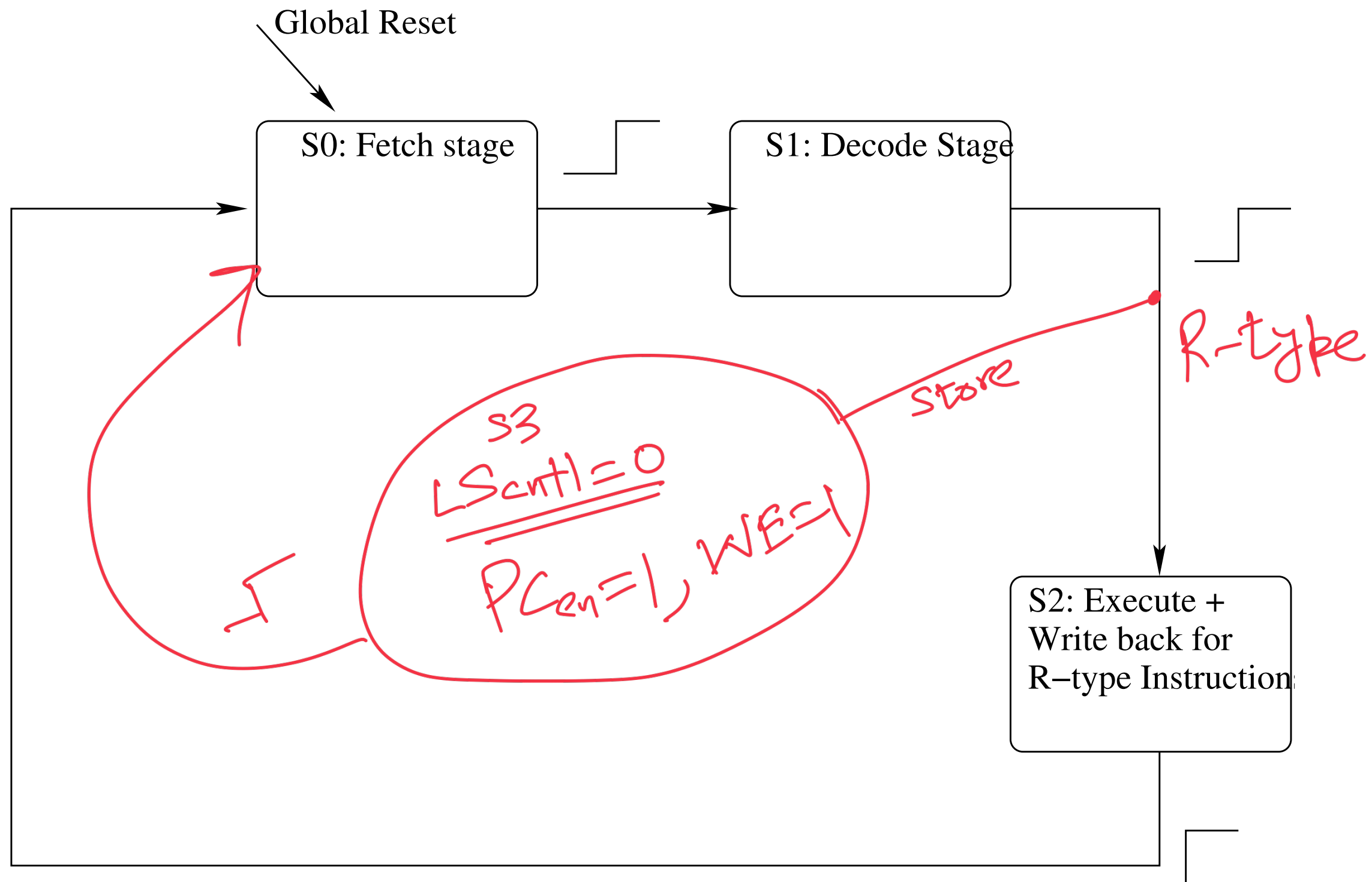

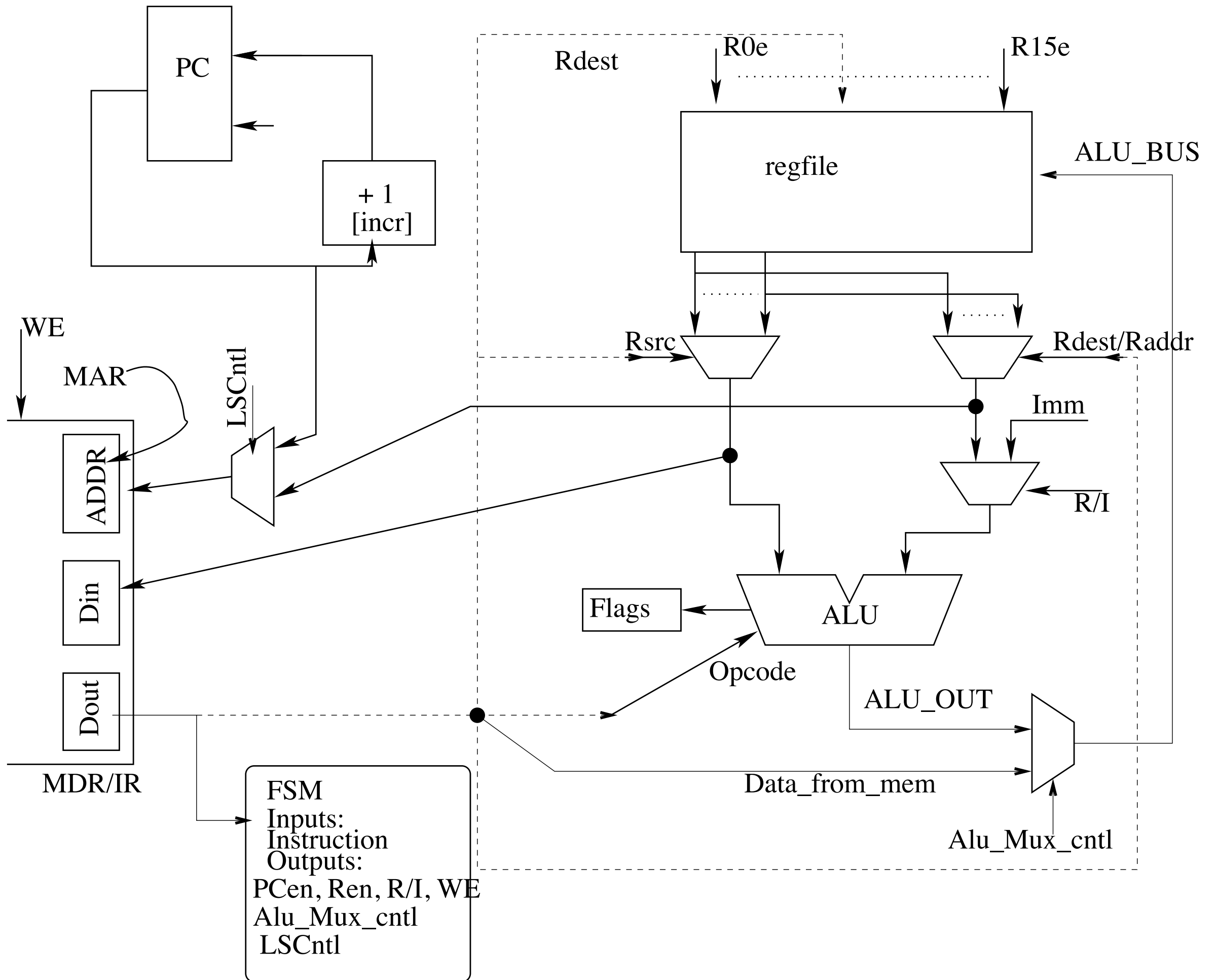


Datapath for Load Instruction

LOAD R_{dest}, R_{addr} , where R_{dest}, R_{addr} in regfile


- Careful about the Opcode and Operand fields in the given instruction set architecture (ISA.pdf)
- In STORE R_{src}, R_{addr} , we have the opcode field $R_{addr} = R_{dest}$ MUX control connection
- In LOAD R_{dest}, R_{addr} , the operand fields (their roles) are sort of reversed. Here $R_{dest} = R_{en}$ (reg_enables) for writing into the regfile.
- Challenge in Load operation:
 - In states S0, S1, DOUT = Fetched instruction [LD R_{dest}, R_{addr}]
 - In state S5, Dout = Data. You may have to “register” from DOUT.
 - You can do it in the data path or in the FSM. [Your job to think about this!!]

FSM for R-type, LOAD, STORE

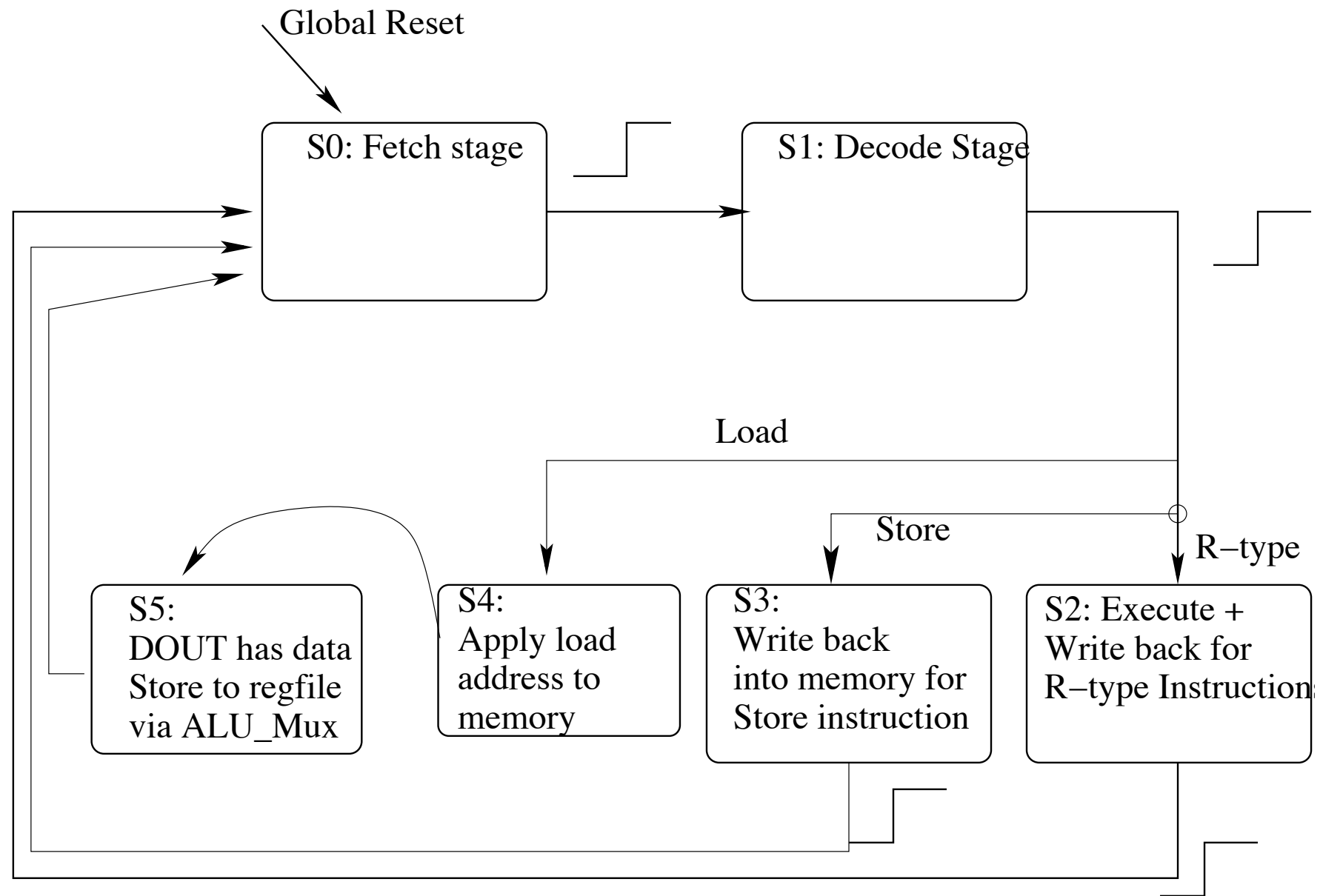


Branch and Jump Instructions

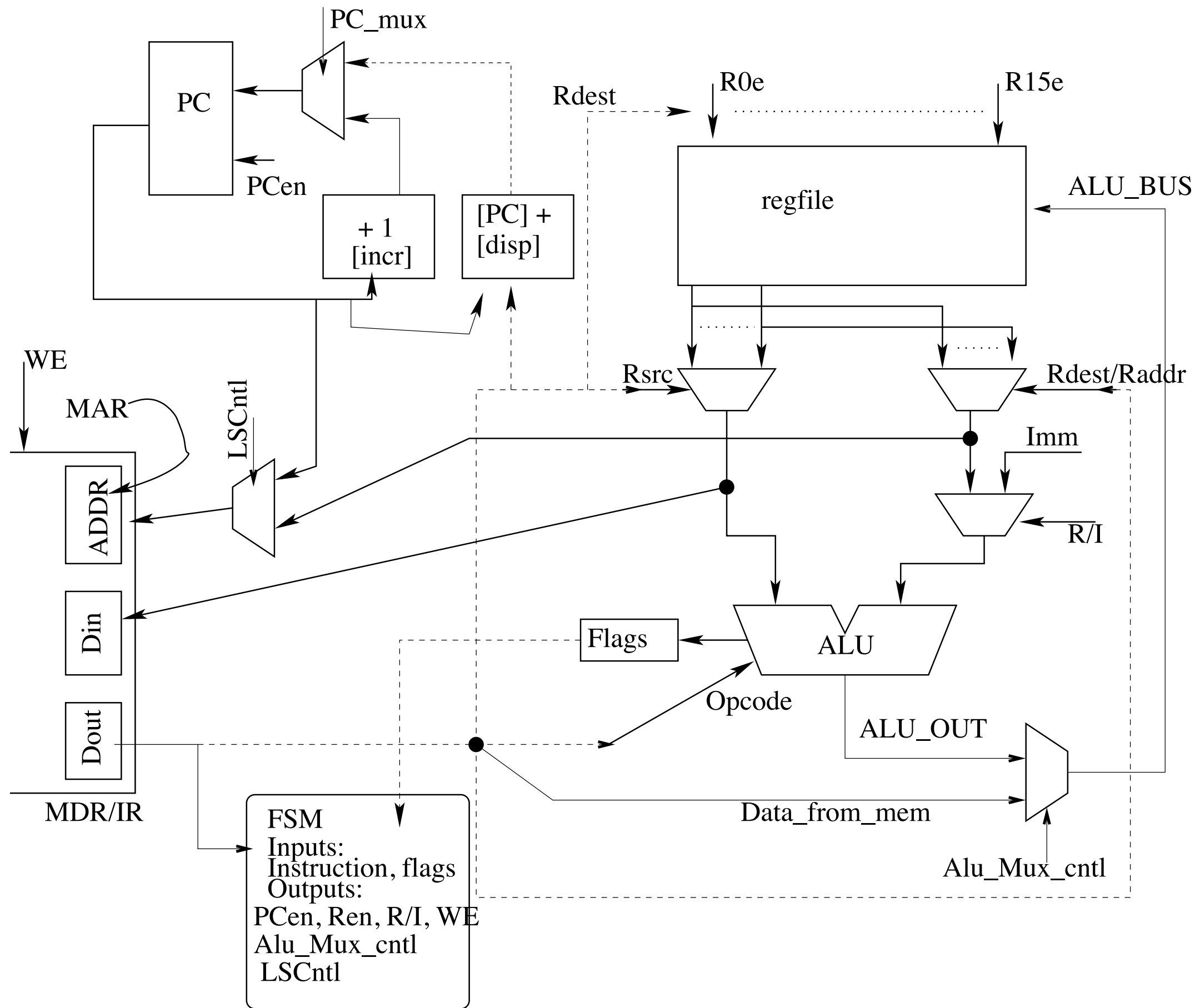- ISA for Branch: *Bcond disp*
 - *cond* = condition codes given in ISA.pdf page 5
 - *disp* = displacement w.r.t. the PC (*disp*=8-bit 2's complement)
- Lets try "*BEQZ disp*":
 - if (Zero-flag == 1) then $PC \leq PC + disp$
- You should do the Jump instruction yourself.



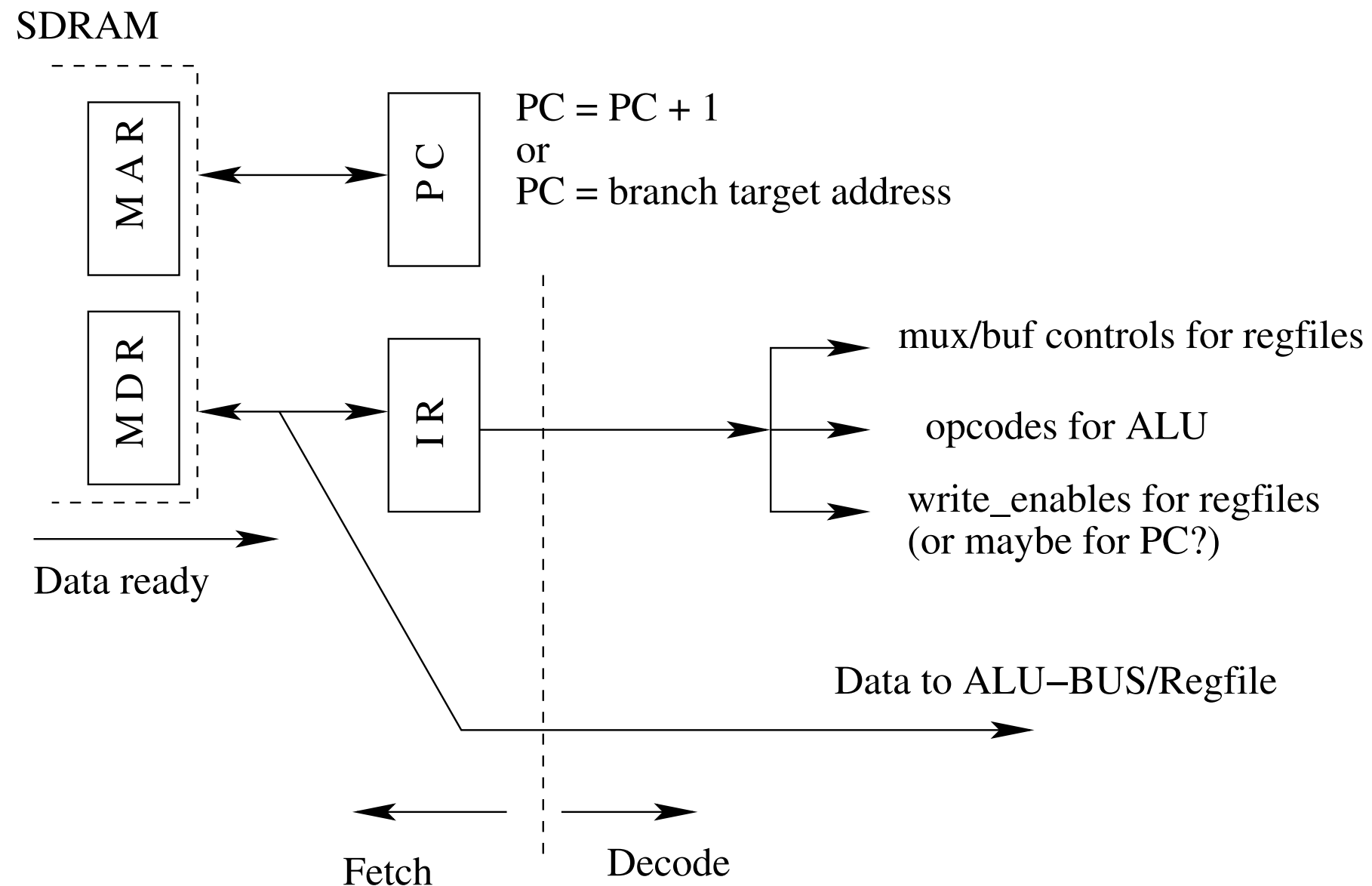The need for an Instruction Register (IR)



Need for an IR

- Needed mostly for a LOAD operation
- DOUT = data_out from memory
 - DOUT holds the instruction, during the instruction fetch cycle
 - DOUT holds DATA to load into regfile, during the data fetch cycle. This data overwrites the instruction, so the R_{dest} , R_{src} , R_{addr} fields get overwritten, and are lost
- To avoid this, use an instruction register (IR), with an IR_enable signal. Copy instruction into IR from DOUT ($[IR] \leftarrow [D_{out}]$) after state $S1$
- In the next slide, see the final data path that accommodates: Load, Store, Reg-to-Reg, Immediate, and branch instructions
- You need to further extend this data path for the Jump instructions

